

# EE236: Lab 1

## Diode Transients & C-V Characteristics of Schottky Diode

Anubhav Bhatla, 200070008

August 22, 2022

### 1 Aim of the experiment

1. To measure and compare the Reverse Recovery Times (RRT) of a P-N Junction diode (1N4007) and a Schottky diode (1N5822).
2. To measure C-V characteristics of a Schottky diode and extract its built-in potential and doping density.

### 2 Design & Working

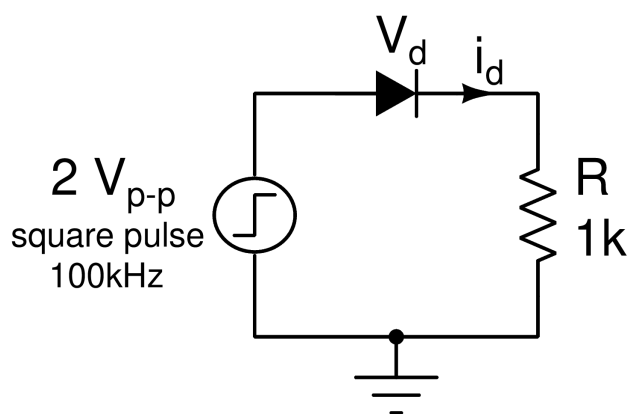


Fig. Circuit to measure Reverse Recovery Time

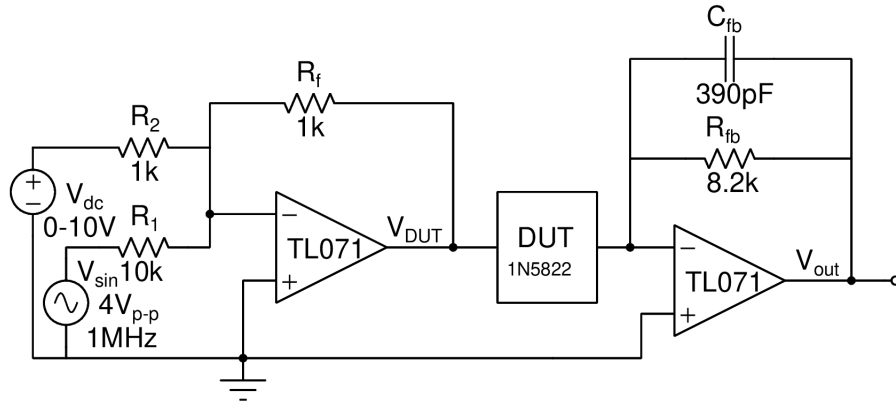


Fig. Circuit to measure Schottky C-V Characteristics

## 3 Simulation

### 3.1 Code Snippet

#### 3.1.1 1N4007 Diode

Reverse Recovery Time for 1N4007

```
.include 1N4007.txt
Vp 1 0 pulse(-1 1 0ns 1ns 1ns 1ms 2ms)
Vdummy 1 2 dc 0
Rd 2 3 100
D 3 0 1N4007
.tran 10ns 3.01ms 2.99ms
.control
run
plot i(Vdummy)
plot v(3)
meas tran tstart MIN_AT i(Vdummy)
meas tran tstop MAX_AT i(Vdummy) from=tstart
print tstop - tstart
.endc
.end
```

### 3.1.2 BAT85 Diode

Reverse Recovery Time for BAT85

```
.include BAT85.txt
Vp 1 0 pulse(-1 1 0ns 1ns 1ns 1ms 2ms)
Vdummy 1 2 dc 0
Rd 2 3 100
X 3 0 BAT85
.tran 10ns 3.00001ms 2.99999ms
.control
run
plot i(Vdummy)
plot v(3)
meas tran tstart MIN_AT i(Vdummy)
meas tran tstop MAX_AT i(Vdummy) from=tstart
print tstop - tstart
.endc
.end
.end
```

## 3.2 Simulation Results

### 3.2.1 1N4007 Diode

Given below is the plot for  $I_D$  waveform for the 1N4007 diode with a 1kHz input pulse, obtained from the transient analysis of the circuit:

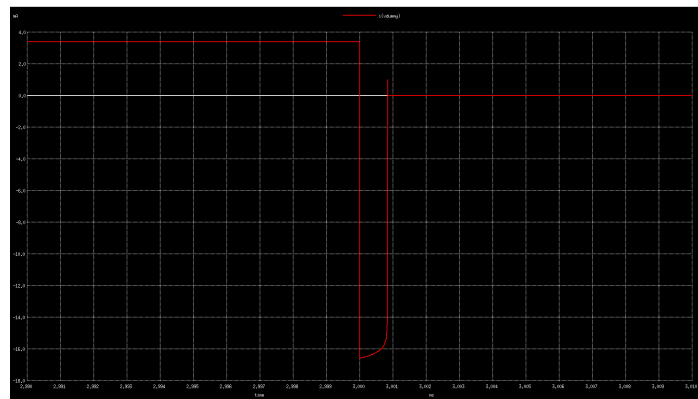


Fig.  $I_D$  plot for 1N4007 Diode at 1kHz

Given below is the plot for  $I_D$  waveform for the 1N4007 diode with a 10kHz input pulse, obtained from the transient analysis of the circuit:

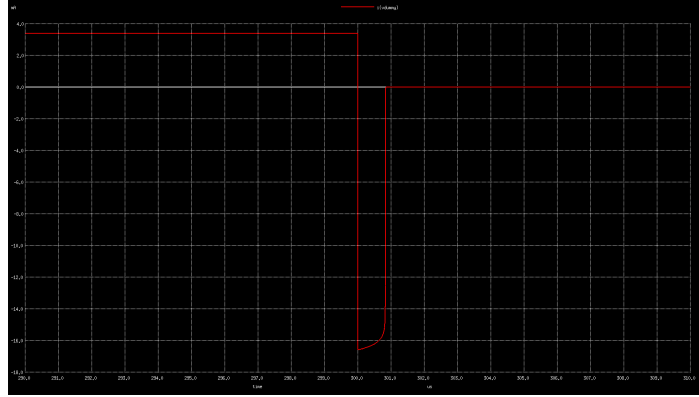


Fig.  $I_D$  plot for 1N4007 Diode at 10kHz

Given below is the plot for  $I_D$  waveform for the 1N4007 diode with a 100kHz input pulse, obtained from the transient analysis of the circuit:

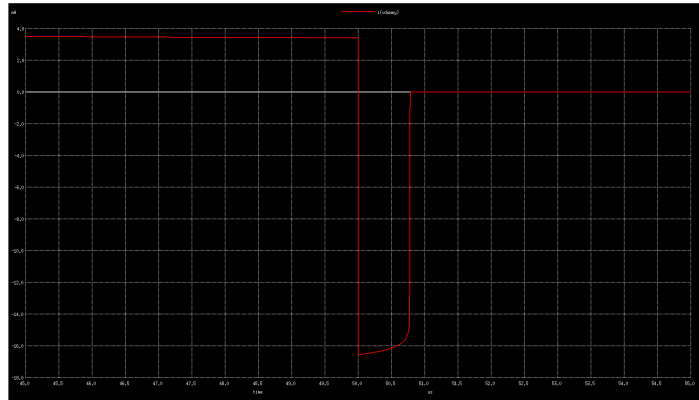


Fig.  $I_D$  plot for 1N4007 Diode at 100kHz

### 3.2.2 BAT85 Diode

Given below is the plot for  $I_D$  waveform for the BAT85 diode with a 1kHz input pulse, obtained from the transient analysis of the circuit:

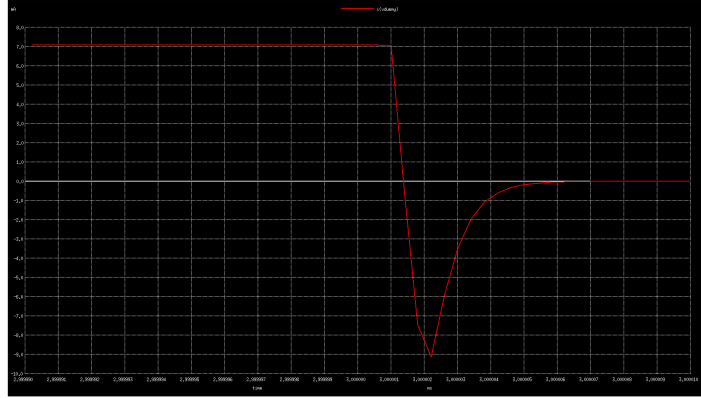


Fig.  $I_D$  plot for BAT85 Diode at 1kHz

Given below is the plot for  $I_D$  waveform for the BAT85 diode with a 10kHz input pulse, obtained from the transient analysis of the circuit:

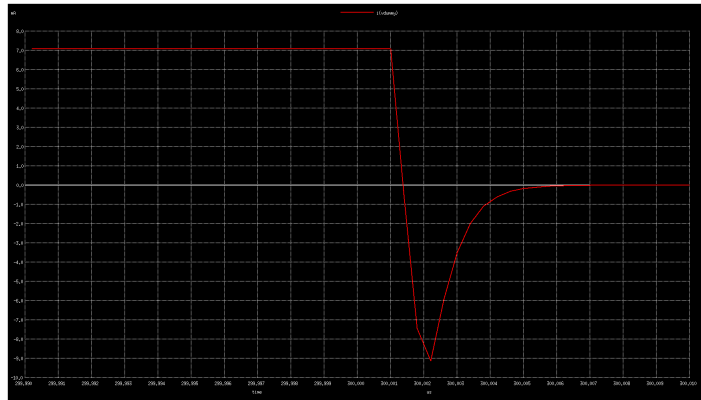


Fig.  $I_D$  plot for BAT85 Diode at 10kHz

Given below is the plot for  $I_D$  waveform for the BAT85 diode with a 100kHz input pulse, obtained from the transient analysis of the circuit:

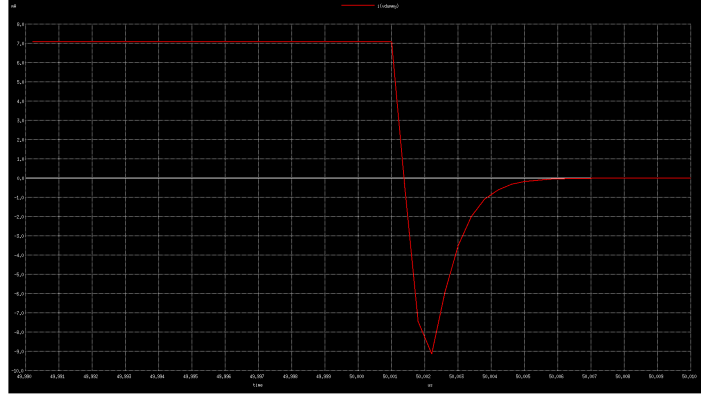


Fig.  $I_D$  plot for BAT85 Diode at 100kHz

Given below are the measured readings using the above simulations for RRT for 1N4007 and BAT85 diodes at various frequencies:

Frequency	RRT of PN	RRT of Schottky
1k	0.84 $\mu s$	8ns
10k	9.99 $\mu s$	7.8ns
100k	4.99 $\mu s$	7.8ns

## 4 Experimental Results

Given below are the measured readings using the above simulations for RRT for 1N4007 and BAT85 diodes at various frequencies:

Frequency	RRT of PN	RRT of Schottky
10k	1.8 $\mu s$	150ns
100k	0.8 $\mu s$	125ns
1M	100ns	110ns
10M	-	-

The capacitance of a Schottky diode can be represented by:

$$\frac{1}{C^2} = \frac{2(V_{bi} - V_i)}{q\epsilon_s\epsilon_o S^2 N_d}$$

The above equation represents a straight line.  $N_d$  can be calculated using the slope whereas  $V_{bi}$  can be calculated using the intercept. For measurement of Schottky diode, the AC gain from  $V_{dut}$  to  $V_{out}$  is given by,

$$\left| \frac{V_{out}}{V_{dut}} \right| = \frac{C_{dut}}{C_{fb}} \frac{1}{\sqrt{1 + \frac{1}{(\omega R_{fb} C_{fb})^2}}}$$

Given below are my observations for the experiment:

$V_{dc}$ (in V)	$V_{out}$	$V_{dut}$	$C_{dut}$
0	40mV	32mV	487.5pF
0.5	48mV	60mV	312.0pF
1	32mV	40mV	312.0pF
1.5	32mV	24mV	520.0pF
2	32mV	24mV	520.0pF
3	32mV	24mV	520.0pF
4	40mV	24mV	520.0pF
5	32mV	24mV	520.0pF
6	32mV	24mV	520.0pF
7	32mV	24mV	520.0pF
8	32mV	24mV	520.0pF
9	32mV	24mV	520.0pF
10	32mV	24mV	520.0pF

Given below are the required plots based on the above readings:

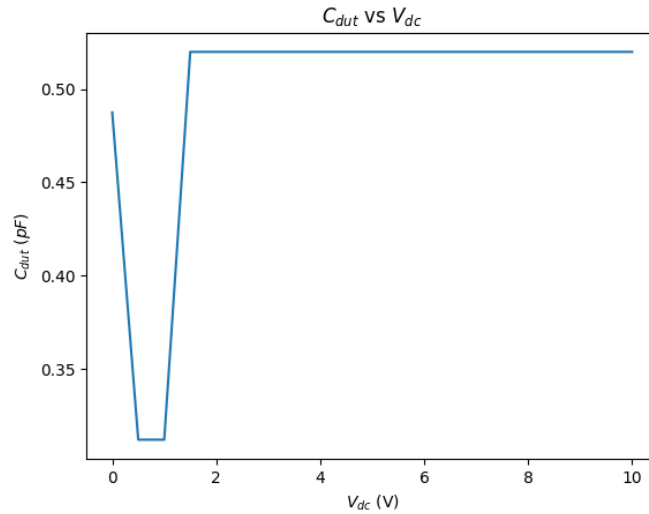


Fig.  $C_{dut}$  vs  $V_{dc}$  Plot for the Schottky diode

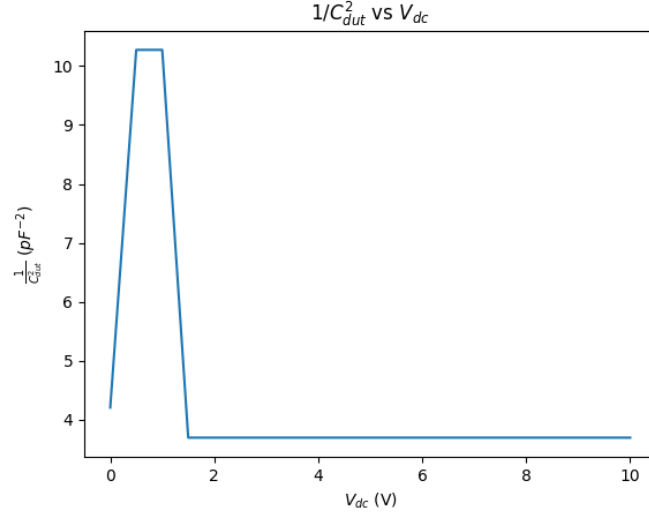


Fig.  $\frac{1}{C_{dut}^2}$  vs  $V_{dc}$  Plot for the Schottky diode

Using the above, I get the value for built-in potential ( $V_{bi}$ ) to be around 0.3V. The area (S) can be calculated using the following equation:

$$I_{rev} = SA^*T^2e^{-V_{bi}/V_t}$$

Using the above equation, I got the value for S to be  $4.145 \times 10^{-8} cm^2$ . To find the doping density, we can use the below formula:

$$Slope = -\frac{2}{q\epsilon_s\epsilon_0 S^2 N_d}$$

Using this we get the value for doping density to be  $5.414 \times 10^{20} cm^{-3}$

## 5 Simulation Exercise

### 5.1 Code Snippet

#### 5.1.1 1N4007 Diode

Bridge Rectifier using 1N4007

```
.include 1N4007.txt
```



```

d1 dummy1 2 1N4007
d2 0 1 1N4007
d3 dummy3 2 1N4007
d4 0 3 1N4007
R1 2 0 1k
Vd1 1 dummy1 dc 0
Vd2 3 dummy3 dc 0
Vin 1 3 sin(0 5 50 0 0)
.tran 0.1m 100m
.control
run
plot v(2) v(1,3)
plot v(2) vs v(1,3)
.endc
.end

```

### 5.1.2 BAT85 Diode

Bridge Rectifier using BAT85

```

.include BAT85.txt
x1 dummy1 2 BAT85
x2 0 1 BAT85
x3 dummy3 2 BAT85
x4 0 3 BAT85
R1 2 0 1k
Vd1 1 dummy1 dc 0
Vd2 3 dummy3 dc 0
Vin 1 3 sin(0 5 50 0 0)
.tran 0.1m 100m
.control
run
plot v(2) v(1,3)
plot v(2) vs v(1,3)
.endc
.end

```

## 5.2 Simulation Results

Given below are the plots for 1N4007 Diode:

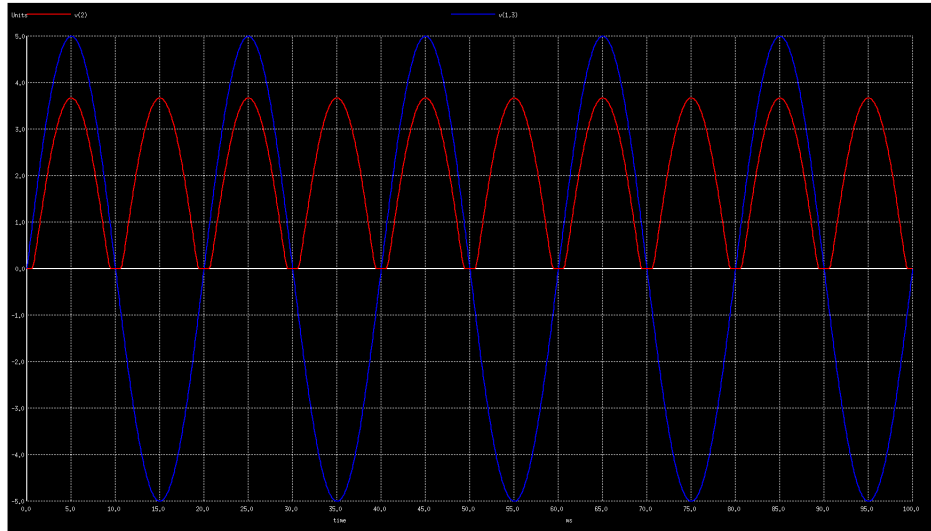


Fig.  $V_{out}$  vs  $V_{in}$  plot for the 1N4007 diode

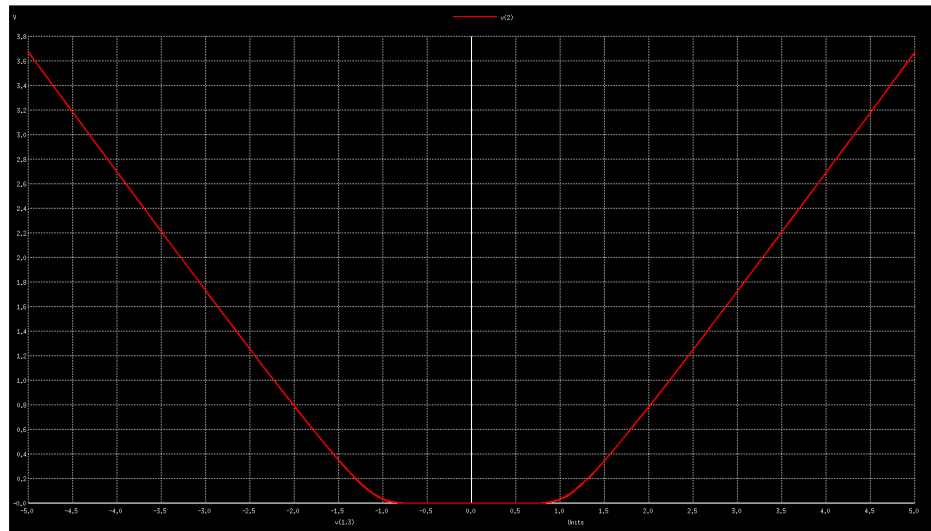


Fig. Transfer characteristics for the 1N4007 diode

Given below are the plots for 1N4007 Diode:

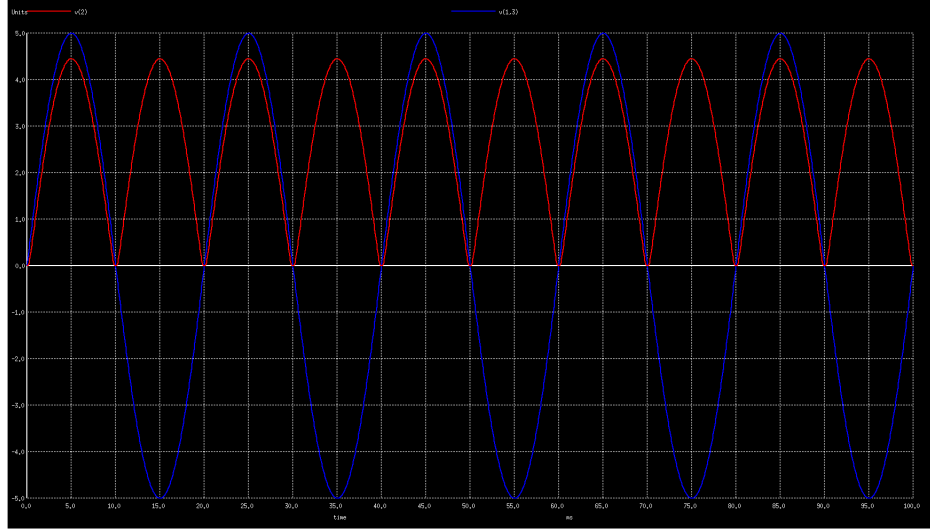


Fig.  $V_{out}$  vs  $V_{in}$  plot for the BAT85 diode

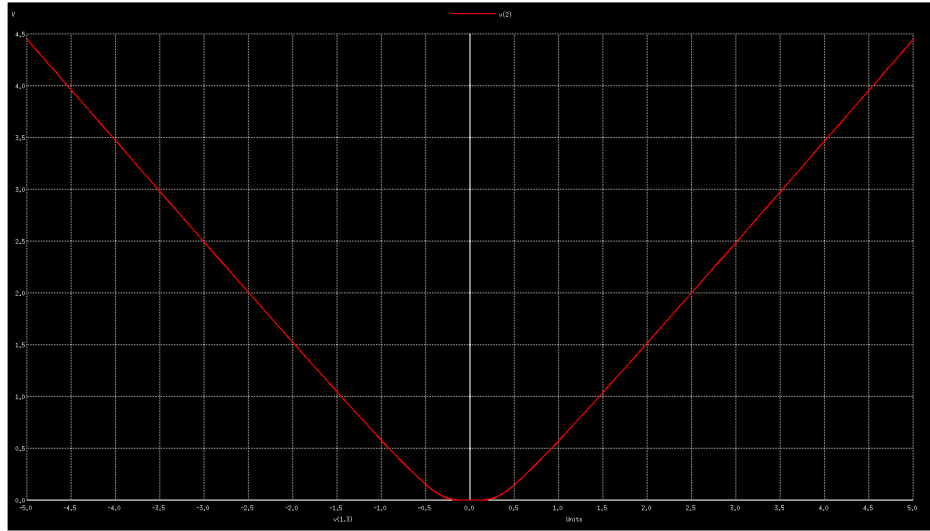


Fig. Transfer characteristics for the BAT85 diode

In these plots we can observe that the drop in  $V_{out}$  compared to the  $V_{in}$  is much less for the BAT85 diode as compared to the 1N4007 diode, due to the smaller voltage drop for BAT85.

Similarly, in the transfer-characteristics plot, we can observe that the region of 0 slope is much smaller for the BAT85 diode, which again implies smaller forward voltage drop for the Schottky diode.

From these observations we can deduce that the **Schottky diode** is a better device for rectification due to its **small forward bias voltage drop**.